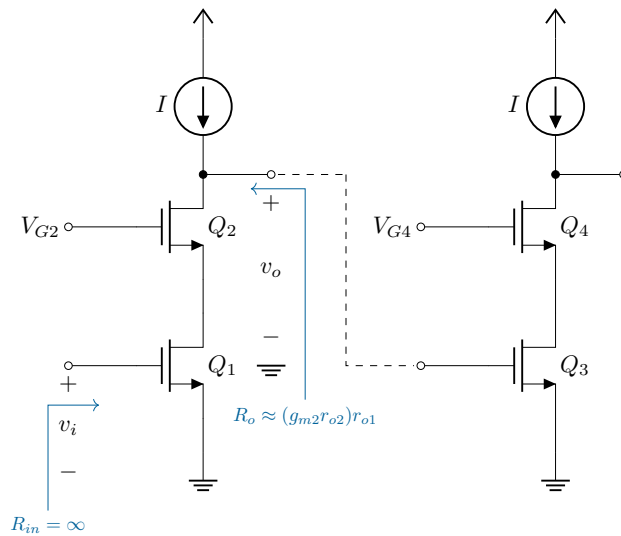


Example 1 + Answer



```

\ctikzset{tripoles/mos style/arrows}
\ctikzset{transistors/arrow pos=end}
\definecolor{highlight}{rgb}{0,0.3843,0.6078}

% Define the start coordinate
\path (0,0) coordinate(IN);

% Draw the main components
\draw (IN) to[short, o-] ++(1,0) node[nmos, anchor=G] (Q1){Q_1};
\draw (Q1.S) to[short] ++(0, -0.5) node[ground] (GND){};

\draw (Q1.D) to[short] ++(0, 0.5) node[nmos, anchor=S] (Q2){Q_2};
\draw (Q2.G) to[short, -o] (IN |- Q2.G) node[left]{V_{G2}};
\draw (Q2.D) to[short, *o] ++(1, 0) coordinate(OUT);
\draw (Q2.D) to[isource, invert, l=I] ++(0, 2) node[vdd]{};

% Draw voltage labels (using CircuiTikZ)
\draw (IN) to[open, v=v_i] (IN |- GND.south);
\draw (OUT) to[open, v=v_o] (OUT |- Q1) node[tlground]{};


% Draw regular labels (using _just_ TikZ)
\draw[->, color=highlight] (IN |- GND.south) ++(-0.3,-0.3)
node[below, scale=0.8]{R_{in} = \infty} -- ++(0,1.55) -- ++(0.75,0);
\draw[->, color=highlight] (OUT |- Q1) ++(0.5,-0.5)
node[below, scale=0.8]{R_o \approx (g_{m2} r_{o2})r_{o1}} -- ++(0,3.1) -- ++(-0.8,0);

% Oh, wait, let's draw another stage!
\draw[dashed] (OUT) ++(0.1,0) -- ++(1,0) coordinate(tmp);
\draw[dashed] (tmp) -- (tmp |- IN) -- ++(1,0) ++(0.1,0) coordinate(IN);

\draw (IN) to[short, o-] ++(1,0) node[nmos, anchor=G] (Q3){Q_3};
\draw (Q3.S) to[short] ++(0, -0.5) node[ground] (GND){};
\draw (Q3.D) to[short] ++(0, 0.5) node[nmos, anchor=S] (Q4){Q_4};
\draw (Q4.G) to[short, -o] (IN |- Q4.G) node[left]{V_{G4}};
\draw (Q4.D) to[short, *o] ++(1, 0) coordinate(OUT);
\draw (Q4.D) to[isource, invert, l=I] ++(0, 2) node[vdd]{};

```

Example 2

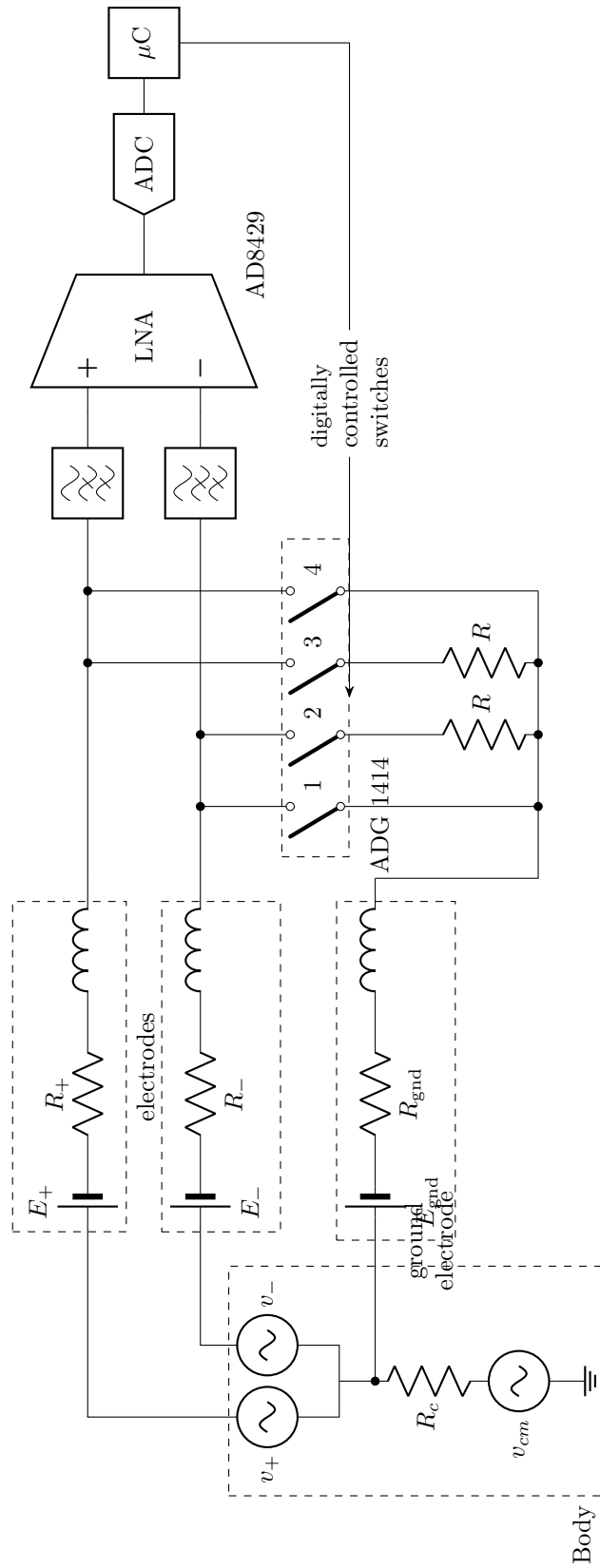

Example 2 Answer

```
\ctikzset{bipoles/cuteswitch/thickness=0.5}

% Draw the source upto the split
\draw (0,0) node[ground](GND0){} to[sV, l=$v_{cm}$] ++(0,1) to [R, l=$R_c$, -*] ++(0,1.5) coordinate(vcm);
\draw (vcm) -- ++(0,0.5) coordinate(diffc);

% Draw the upper/+ path including the LNA
\draw (diffc) -- ++(-0.5, 0) -- ++(0, 0.5) to[sV, l=$v_+$, name=vplus] ++(0,1)
  -- ++(0, 2) -- ++(2.5, 0) coordinate(skin+ a);
\draw (skin+ a) to[battery2, l=$E_+$, name=eplus] ++(1,0) to[R=$R_+$, name=rplus] ++(2,0) to[L, name=lplus] ++(2,0);
\draw (skin+ b) -- ++(0.5,0) -- ++(4,0) coordinate(hpin+);
\draw (hpin+) to[highpass] ++(2,0) node[inst amp, anchor=+, noinv input up, circuitikz/amplifiers/scale=1.6,

% Define the coordinate to align the -/lower path.
\coordinate (skin- a) at (LNA.- -| skin+ a);

% Draw the lower path
\draw (diffc) -| ++(0.5,0.5) to[sV,l_=$v_-$, name=vminus] ++(0, 1) |- (skin- a);
\draw (skin- a) to[battery2, l_=$E_-$, name=eminus] ++(1,0) to[R, l_=$R_-$, name=rminus] ++(2,0) to[L, name=lminus] ++(2,0);

% Define the ground coordinate to align the lowest path
\coordinate (gnd a) at (vcm -| skin+ a);
\draw (vcm) -- (gnd a) to[battery2, l_=$E_{\mathrm{gnd}}$, name=egnd] ++(1,0) to[R, l_=$R_{\mathrm{gnd}}$, name=rgnd] ++(2,0);

% switch set
\def\swdown{-3.2}
\draw (skin- b) ++(1,0) coordinate(sw1);
\draw (sw1) to[cosw, invert, mirror, l=1, *-, name=s1] ++(0,\swdown) to[short, -*] ++(0, -1.5);
\draw (sw1) ++(1,0) coordinate(sw2);
\draw (sw2) to[cosw, invert, mirror, l=2, *-, name=s2] ++(0,\swdown) to[R=$R$, -*] ++(0, -1.5);
\draw (sw2|-skin+ b) ++(1,0) coordinate(sw3);
\draw (sw3) to[short, *-, name=s3] (sw3|-sw2) to[cosw, invert, mirror, l=3,] ++(0,\swdown) to[R=$R$, -*] ++(0, -1.5);
\draw (sw3) ++(1,0) coordinate(sw4);
\draw (sw4) to[short, *-, name=s4] (sw4|-sw2) to[cosw, invert, mirror, l=4, name=s4] ++(0,\swdown) to[short] ++(0, -1.5);
\draw (gnd b) |- (endsw);

% boxes (use fit library from TikZ)
\node[rectangle, draw, dashed, fit=(GND0) (vplus) (vpluslabel) (vminuslabel)](body) {};
\node[anchor=south east, align=center] at (body.south east) {Body};

\node[rectangle, draw, dashed, fit=(rplus) (eplus) (epluslabel) (rpluslabel) (lplus)](top) {};
\node[rectangle, draw, dashed, fit=(eminus) (rminus) (eminuslabel) (rminuslabel) (lminus)](bot){};


\node[anchor=center, align=center] at (($top.south)!0.5!(bot.north)$) {electrodes};
\node[rectangle, draw, dashed, fit=(egnd) (rgnd) (egndlabel) (rgndlabel) (lgnd)](gnd){};

\node[below, align=center] at (gnd.south) {ground\\ electrode} ;
\node[rectangle, draw, dashed, fit=(s1) (s4label), inner ysep=8pt](switches){};

% ADC and micro
\draw (LNA.out) -- ++(0.5,0) node[msport,circuitikz/RF/scale=2] (ADC){ADC};
\draw (ADC.right) -- ++(0.5,0) node[twoportshape, anchor=left, t=$\mu$C](uC){};
\draw (uC.south) -- (uC.south |- switches.east) -- ++(-4,0) node[align=left, anchor=east] (DCS){\small digitally};
\draw[-Stealth] (DCS.west) -- (switches.east);

\node [anchor=north west] at ([xshift=-10pt, yshift=-5pt]switches.south east) {ADG 1414};
\node [anchor=north west] at ([yshift=-5pt]LNA.refv down) {AD8429};
```

Challenge

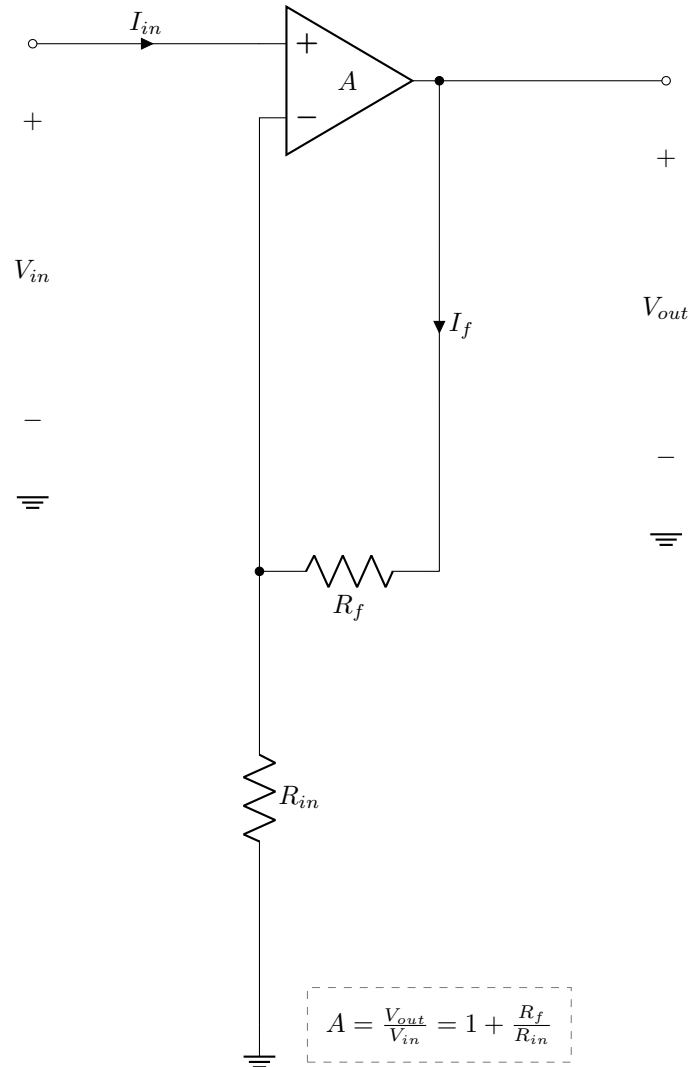

Challenge Answer

```
\path (0,0) coordinate(IN);

\draw (IN) to[short, o-, i=${I_{in}}] ++(1,0) node[op amp, noinv input up, anchor=+](opamp){$A$};
\draw (opamp.-) to[short, -*] ++(0,-2) coordinate(c) to[R, l=${R_{in}}] ++(0,-2) node[ground](g){};
\draw (c) to[R, l=${R_f}] (opamp.out |- c) (opamp.out) to[short, *-, i=${I_f}] (opamp.out |- c);
\draw (opamp.out) to[short, -o] ++(1,0) to[open, v=${V_{out}}] ++(0,-2) node[tlground]{};
\draw (IN) to[open, v=${V_{in}}] ++(0,-2) node[tlground]{};


\draw (opamp.out |- g) node[] (t){$A = \frac{V_{out}}{V_{in}} = 1 + \frac{R_f}{R_{in}}$};

\node[rectangle, draw, dashed, color=gray, fit=(t)]{};
```

EE BSC specific

By \sqrt{KS}

DCM

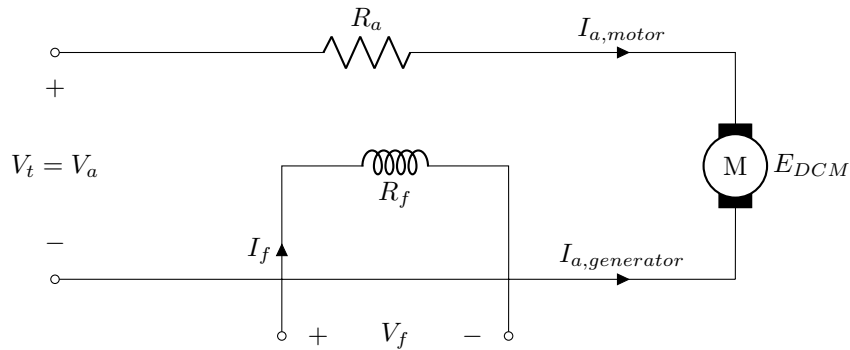

```
% Defining the input node
\coordinate (IN) at (0,0);
\coordinate (FCircuit) at (2,-2.5);
\draw
(IN) to [short, o-] ++(1.5,0)

% Drawing resistor
to[R, l=$R_a$] (4,0)

% Drawing motor current
to[short, -, i^={$I_{a, motor}$}] ++(2,0)
to[sV, color=white, name=M1, l=$E_{DCM}$] ++(0,-2)


% Drawing OC at input
(IN) to [open, v^>={$V_t}=V_a$] ++(0,-2)
to[short, o-] ++(4,0)
to[short, i^={$I_{a, generator}$}] ++(2, 0)

++(0,1) node[elmech](motor){M} ++(0, -1)

(FCircuit) to[short, i^={$I_f$}, o-] ++(0,1.5)
to[short, -] ++(0.5,0)
to[L, l=$R_f$] ++(1,0)

to[short, -] ++(0.5,0)
to[short, -o] ++(0,-1.5)
(FCircuit) to [open, v^>={$V_f$}] ++(2,0);
```

PMSM

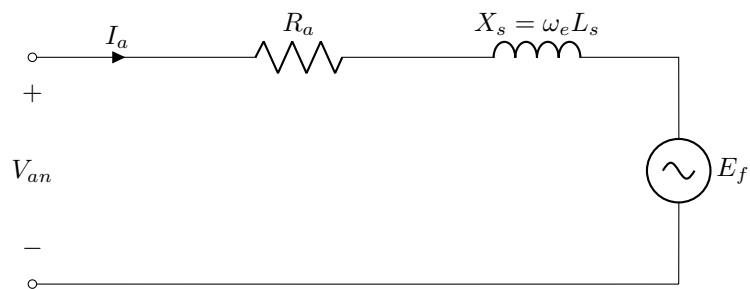

```

\centering
% Input node
\coordinate (IN) at (0,0);
\draw
(IN) to [short,o-,i^=${I_a}$] ++(1.5,0)

% Resistor
to[R, l=${R_a}$] ++(1.7,0)


% Inductor
to[american inductor, l=${X_s}=\omega_e L_{s}$] ++(2.5,0)

% Wire and source
to [sV, l=${E_f}$] ++(0,-2) coordinate(E_f_out)

% Horizontal wire bottom
(0, -2) to[short,o-] (E_f_out)
(IN) to [open, v^>=${V_{an}}$] (0,-2);

```

IM

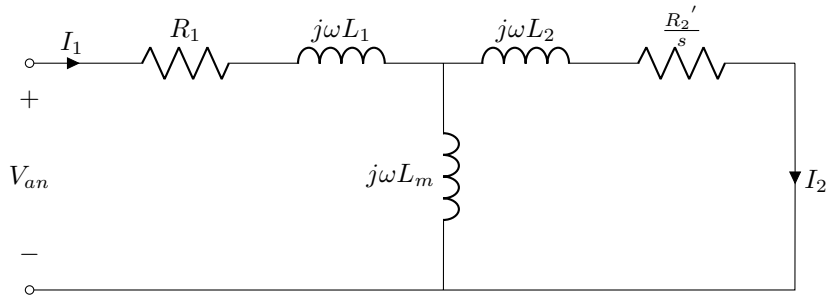

```

\coordinate (IN) at (0,0);

\draw
% Resistor and terminal 1
(IN) to [short,o-,i^=  $I_1$ ] ++(0.75,0)
to[R, l= $R_1$ ] ++(1.25,0)
to[american inductor, l= $j\omega L_1$ ] ++(1.5,0)

% Resistor and terminal 1
(3.5,0) to [short,-] ++(0.25,0)

to[american inductor, l= $j\omega L_2$ ] ++(1.25,0)
to[R, l= $\frac{R_2}{s}$ ] ++(1.5,0)
to [short,-] ++(0.25,0)

% Vertical traces
(6.75,0) to [short,-,i^= $I_2'$ ] (6.75,-2)
to [short,-o] (0,-2)

(3.65,0) to[american inductor, l= $j\omega L_m$ ] ++(0,-2)

(IN) to [open, v^= $V_{an}$ ] (0,-2);

```